



02

CHAPTER

BIOPHYSICS LECTURE (2)

المحاضرة الثانية

TOPICS

- 1 Coulomb's Law
- 2 Ohm's Law
- 3 SERIES CIRCUIT RESISTANCE
- 4 Series Circuit Voltage and Current
- 5 Parallel Circuits



Scientific content prepared by
Booknerd Team



01092318718

DENT - 6 OCT






Coulomb's Law

Coulomb's Law

$$F = K \frac{q_1 q_2}{r^2}$$

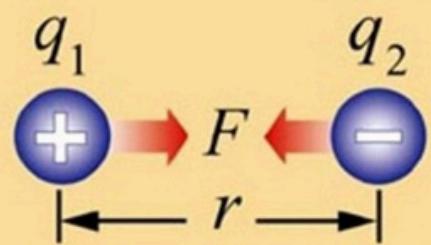
Force (N) Constant $(9 \times 10^9 \text{ N} \cdot \text{m}^2/\text{C}^2)$ Charges (C) Distance (m)



- Coulomb's law relates the **force** between two single charges separated by a distance.

Current


- Electricity** is the flow of electrons in a conductor from one atom to the next atom in the same general direction.
- This flow of electrons is referred to as **current** and is designated by the symbol "I".
- Current is measured in **amperes**, which is often shortened to "amps". The letter "A" is the symbol for amps.
- Current that constantly flows in the same direction is called **direct current (DC)**. Current that periodically changes direction is called **alternating current (AC)**.

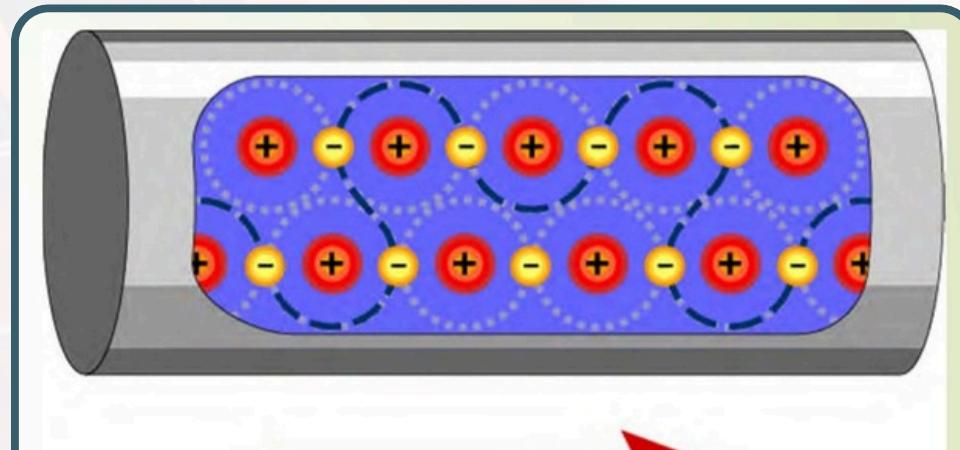

| Commonly Used Units | | |
|---------------------|------------|---------------|
| Unit | Short Form | Decimal Value |
| 1 kiloampere | 1 kA | 1000 A |
| 1 ampere | 1 A | 1 A |
| 1 milliampere | 1 mA | 0.001 A |
| 1 microampere | 1 μ A | 0.000001 A |

Voltage

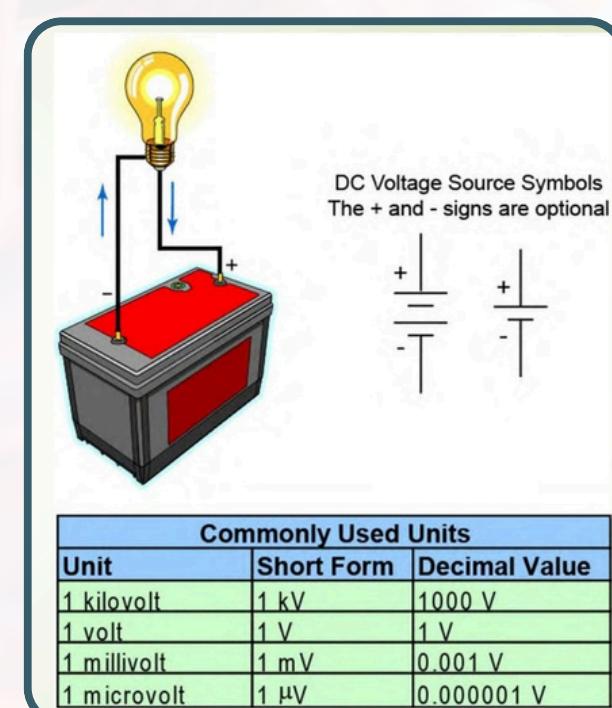
- The force that causes current to flow through a conductor is called a **difference in potential**, **electromotive force (emf)**, or **voltage**.
- Voltage is designated by the letter "E" or the letter "V." The unit of measurement for voltage is **volts** which is also designated by the letter "V."






Voltage

- All voltage sources share the characteristic of an excess of electrons at one terminal and a shortage at the other terminal.
- This results in a difference of potential between the two terminals.
- For a DC voltage source, the polarity of the terminals does not change, so the resulting current constantly flows in the same direction.
- The terminals of an AC voltage source periodically change polarity, causing the current flow direction to change with each switch in polarity.

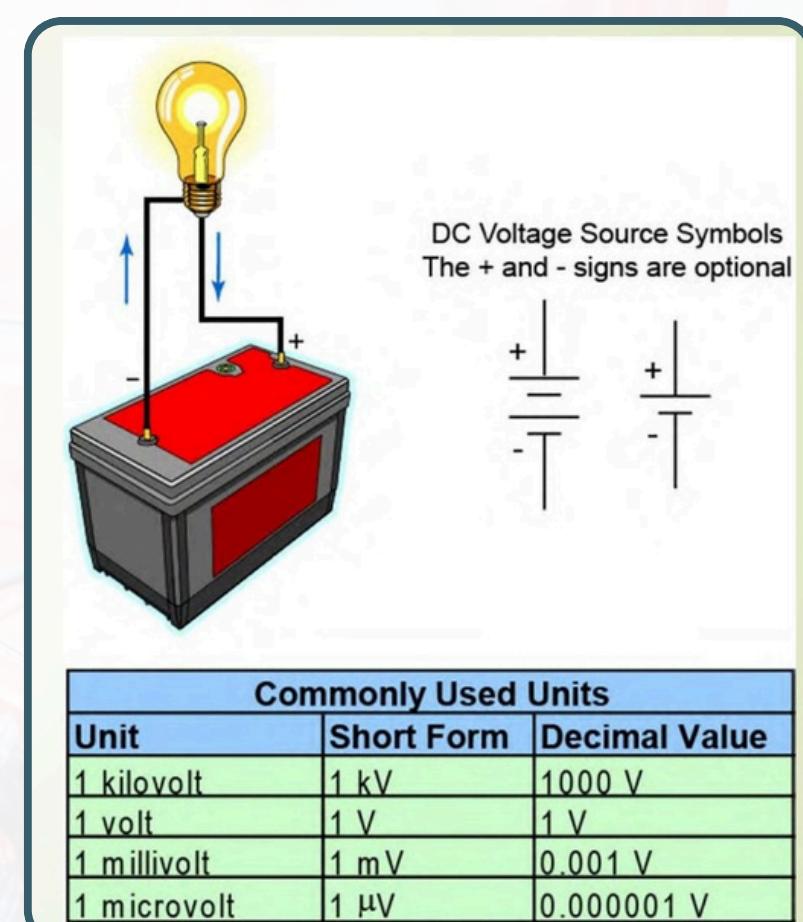


Resistance

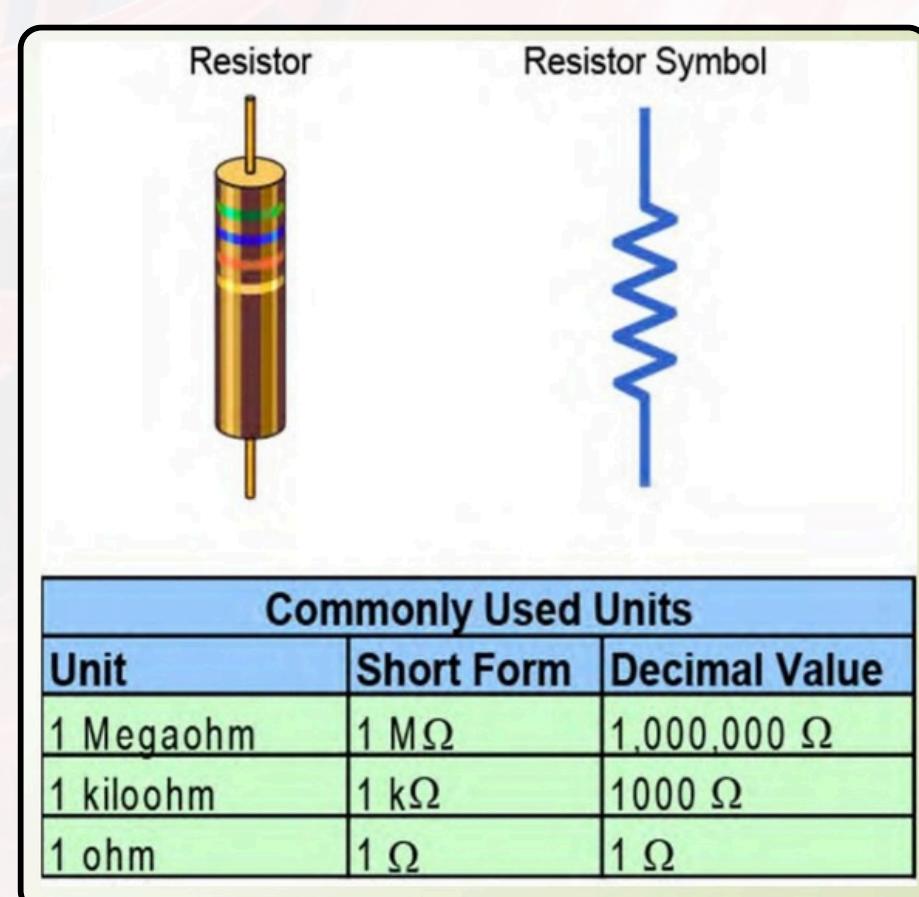- A third factor that plays a role in an electrical circuit is resistance. Resistance is the property of a circuit, component, or material that opposes current flow.
- All material resists the flow of electrical current to some extent.
- Resistance is designated by the symbol “R.” The unit of measurement for resistance is the ohm, symbolized by the Greek letter omega Ω .





Ohm's Law

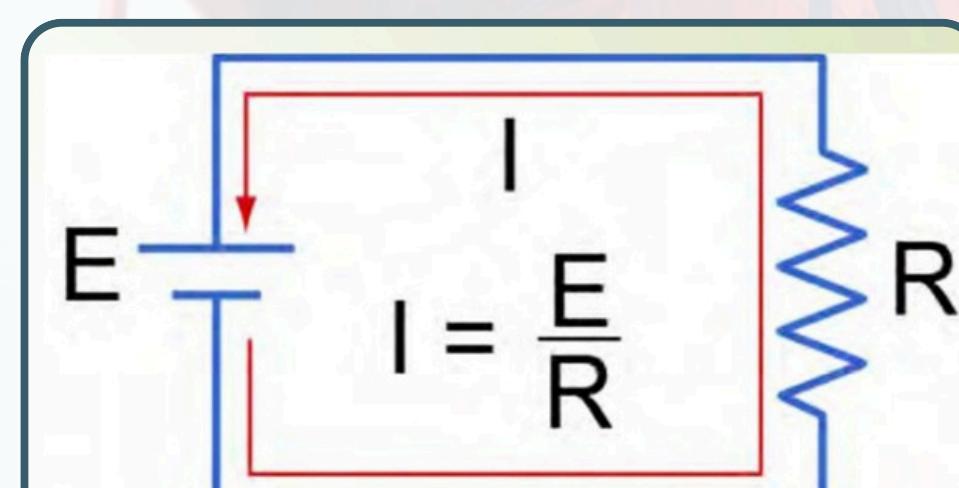

Current (I) is measured in amperes (amps)
 Voltage (E) is measured in volts
 Resistance (R) is measured in ohms

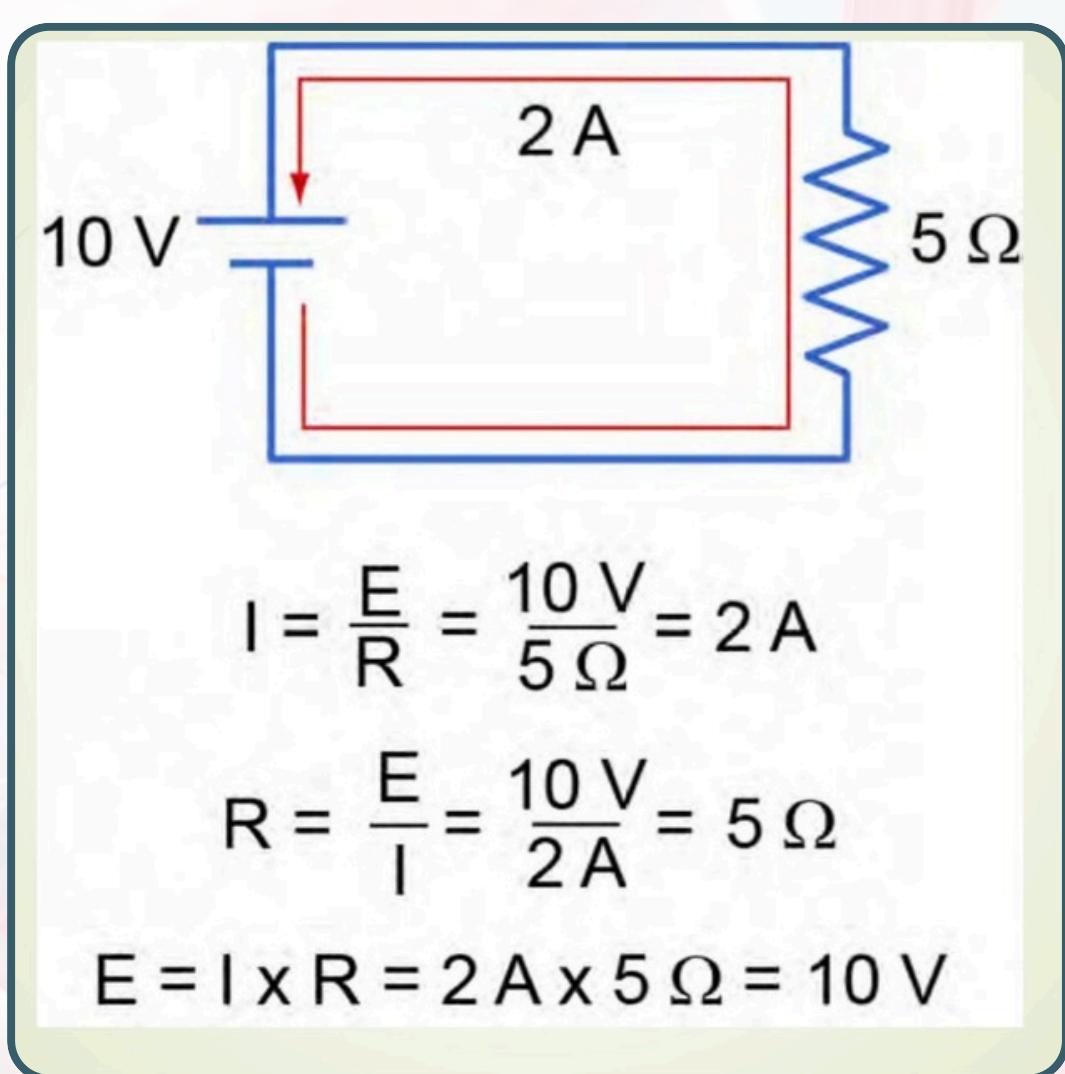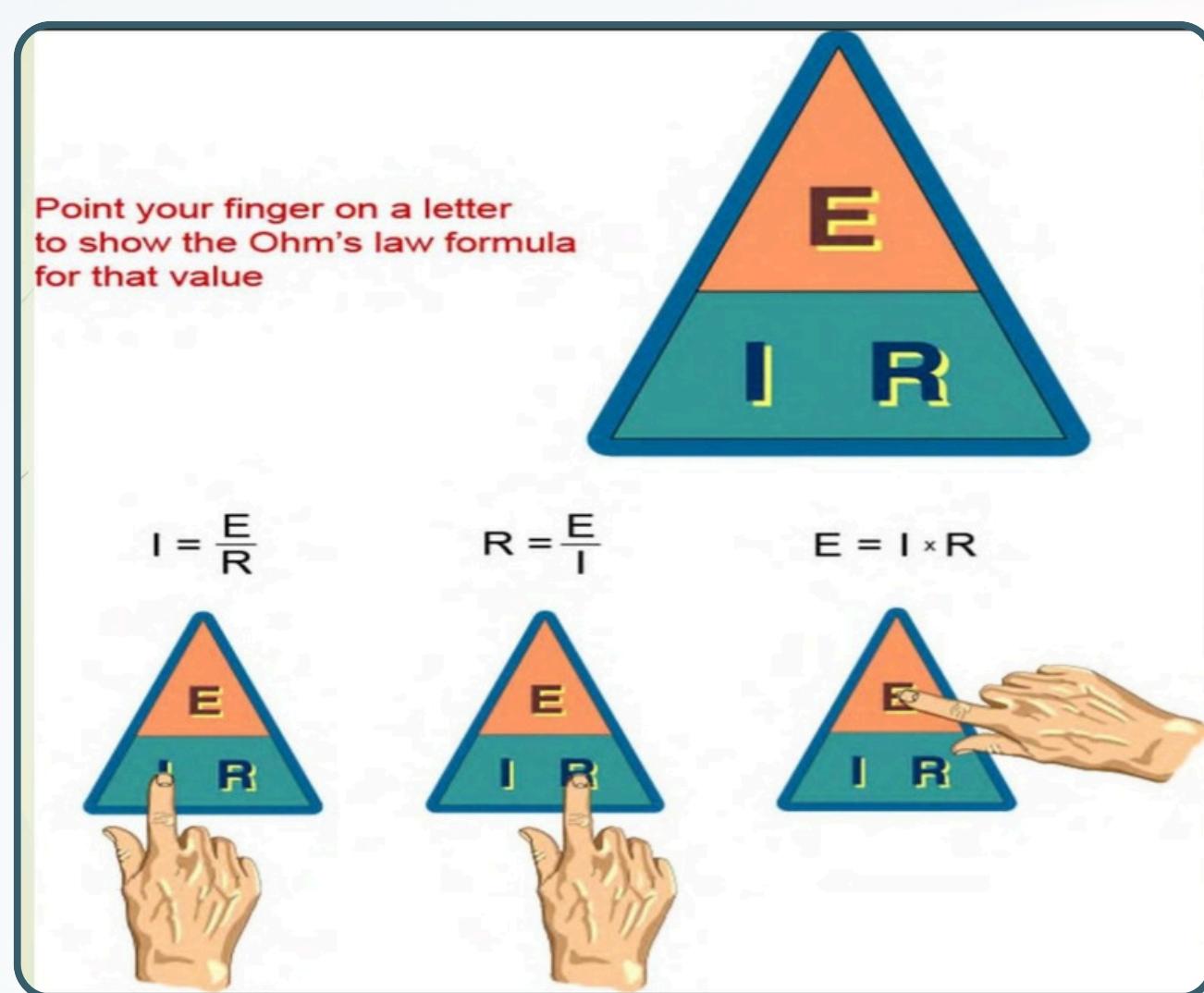
- A simple electric circuit consists of a voltage source, some type of load, and conductors to allow electrons to flow between the voltage source and the load.
- Ohm's law defines the relationship between current, voltage, and resistance and shows that current varies directly with voltage and inversely with resistance.





Series Circuit Resistance

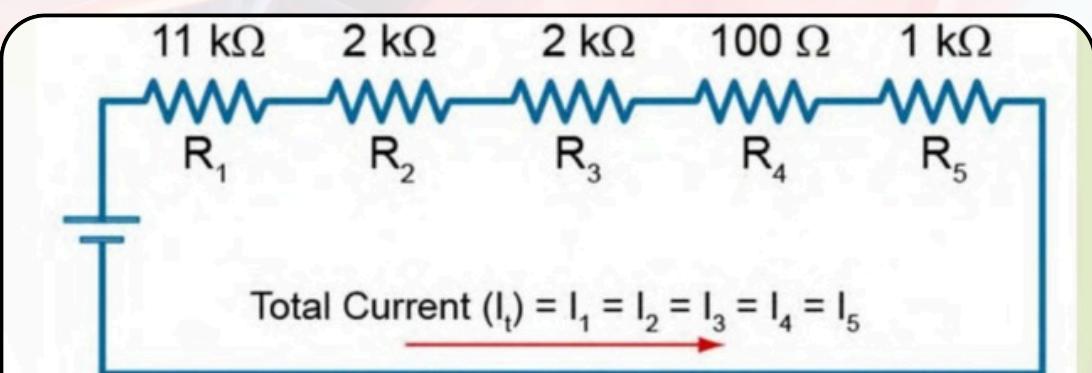- A series circuit is formed when any number of resistors are connected end-to-end so that there is only one path for current to flow.**



$$\text{Total Resistance} = R_t = R_1 + R_2 + R_3 + R_4 + R_5$$


$$R_t = 11,000 \Omega + 2000 \Omega + 2000 \Omega + 100 \Omega + 1000 \Omega$$

$$R_t = 16,100 \Omega = 16.1 \text{ k}\Omega$$

| Commonly Used Units | | |
|---------------------|------------|---------------|
| Unit | Short Form | Decimal Value |
| 1 Megaohm | 1 MΩ | 1,000,000 Ω |
| 1 kilohm | 1 kΩ | 1000 Ω |
| 1 ohm | 1 Ω | 1 Ω |

Series Circuit Voltage and Current


- The current in a series circuit can be determined using Ohm's law.
- First, total the resistance, and then divide the source voltage by the total resistance.
- This current flows through each resistor in the circuit.
- The voltage measured across each resistor can be calculated using Ohm's law.
- The voltage across a resistor is often referred to as a voltage drop. The sum of the voltage drops across each resistor is equal to the source voltage.

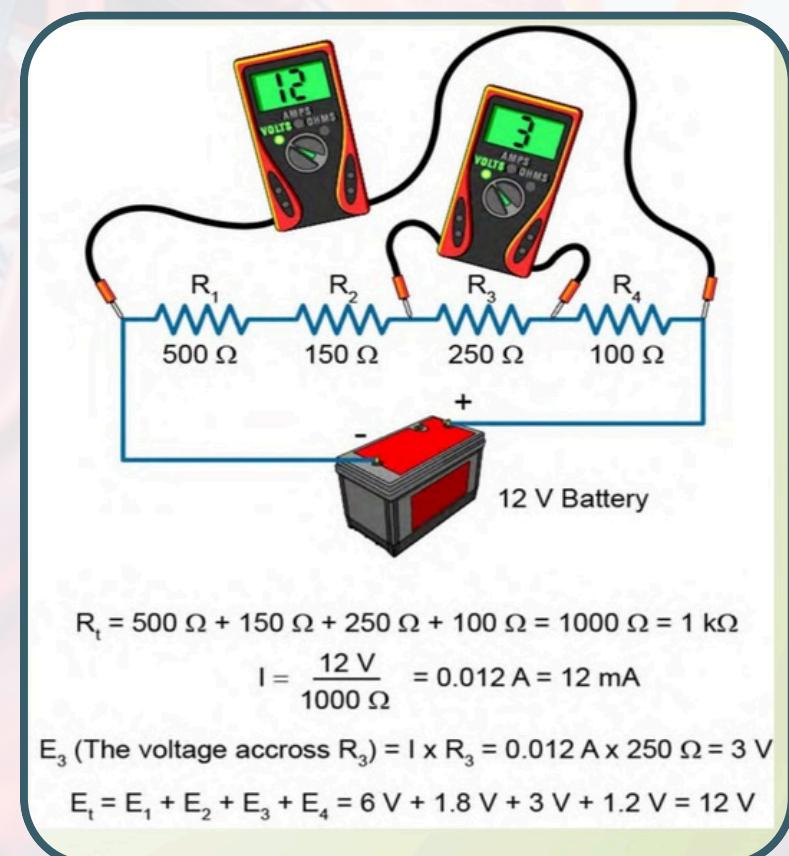




Parallel Circuits

- A parallel circuit is formed when two or more resistances are placed in a circuit side-by-side so that current can flow through more than one path.
- There are two paths of current flow.
- One path is from the negative terminal of the battery through R_1 returning to the positive terminal.
- The second path is from the negative terminal of the battery through R_2 returning to the positive terminal of the battery.


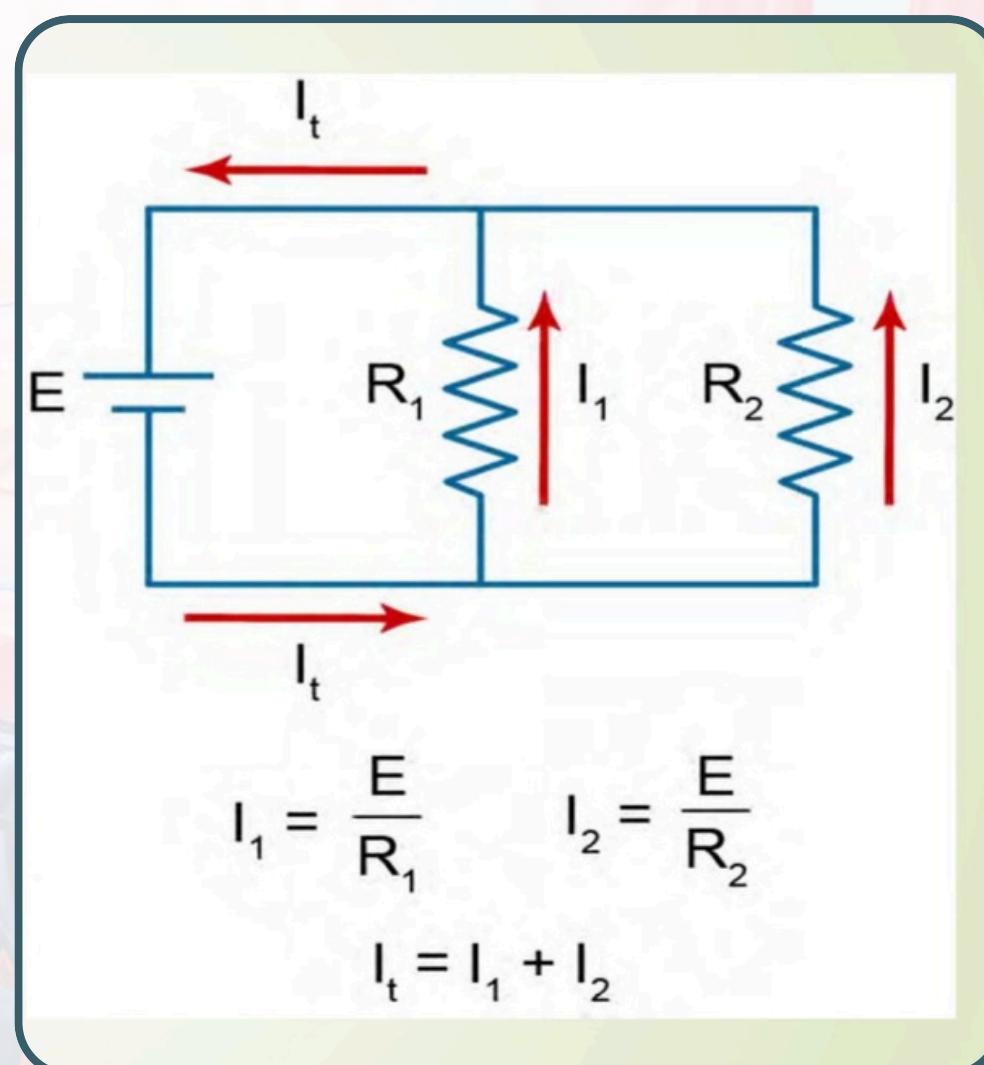


Examples

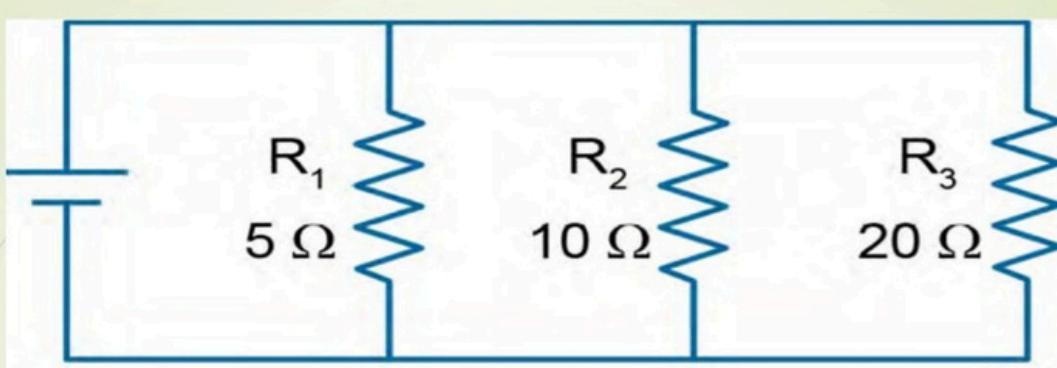

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} =$$
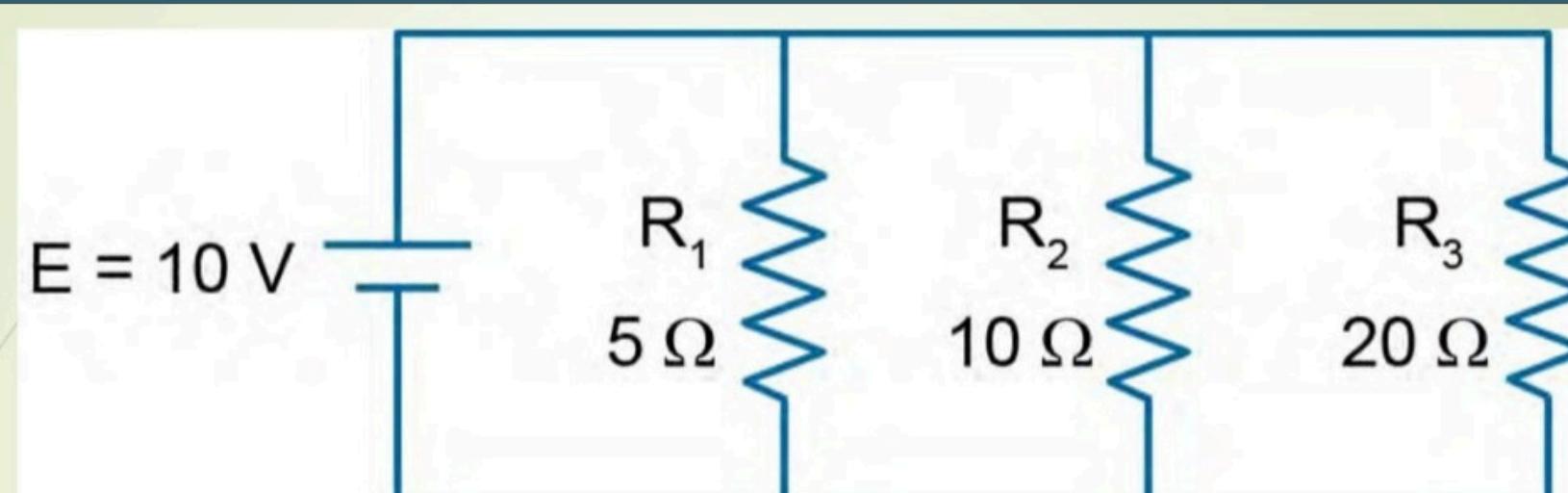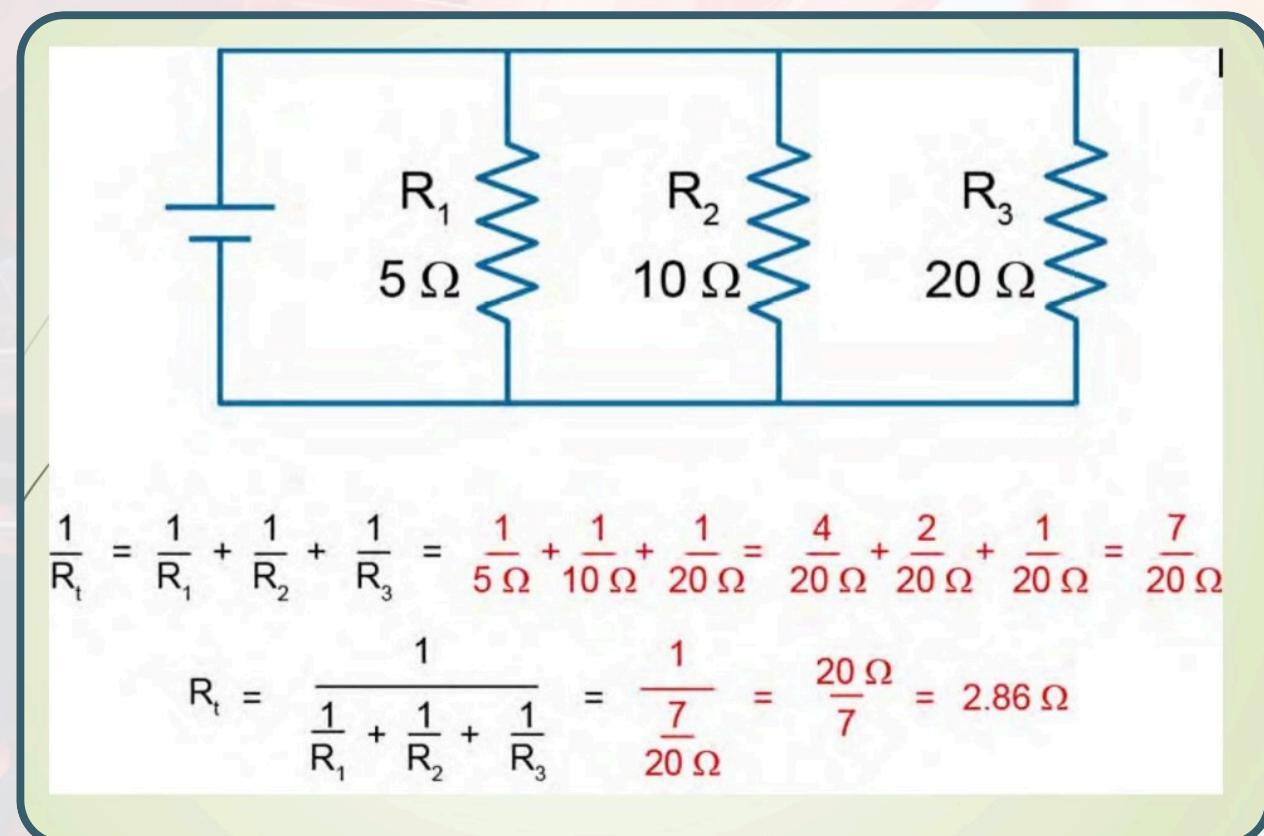
$$R_t = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} =$$



$$I_t = I_1 + I_2 + I_3 = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3} = \frac{10\text{ V}}{5\Omega} + \frac{10\text{ V}}{10\Omega} + \frac{10\text{ V}}{20\Omega} = 2\text{ A} + 1\text{ A} + 0.5\text{ A} = 3.5\text{ A}$$

$$I_t = \frac{E}{R_t} = \frac{10\text{ V}}{2.86\Omega} = 3.5\text{ A}$$

